



MONASH University

Monash University

ECE2072

Assignment Report

Processor in Verilog HDL

Loo Yi Ren Dillon (33455953)
10-16-2023

Contents

Contents	1
Introduction	2
Components	2
Sign Extender.....	2
Tick Counter	2
ALU	3
Register	3
Multiplexer.....	4
Resource usage and timing analysis	4
Design & implemented Datapath	5
Arithmetic	6
Display	6
Bit-shifting.....	7
Move immediate	7
Product testing	8
Sign Extender testbench.....	8
Tick Counter testbench	8
ALU testbench	8
Multiplexer testbench.....	9
Register testbench	9
Processor testbench	9
Conclusion	9
Appendix A: Verilog modules	10

Introduction

This formal report presents process of designing and coding a processor using Verilog. Building a processor is a fundamental task in computer engineering, involving intricate work in digital logic design and control implementation. This report provides a detailed account of the project, outlining the decisions made, challenges encountered, and innovative solutions developed throughout the journey. The objective is to gain a deeper understanding of processor architecture and strengthen coding skills while contributing to the field of digital systems.

Components

Sign Extender

 


Figure 1: high level diagram of sign extender module.

The sign extender module serves the role of expanding the 9-bit input of the processor into a 16-bit binary representation, accommodating both positive and negative 2's complement numbers. It's operation involves analysing the most significant bit (MSB) of the input and replicating it six times to the left, thereby generating the extended 16-bit output.

Tick Counter

 


Figure 2: high level diagram of ALU module.

Table 1: encoding table for tick counter.

States	Encoding
state 1	0001
state 2	0010
state 3	0100
state 4	1000

The tick counter is a finite state machine that maintains the current state of the processor. It consists of 4 states following the one hot encoding to represent each state. It updates to next state accordingly during each clock if the enable pin is turned on. If reset pin is on, the tick counter will return to the 0th state during the next positive edge of the clock.

ALU

 


Figure 3: high level diagram of ALU module.

The arithmetic logic unit (ALU) is the component that performs arithmetic operations for the processor, including:

- Addition
- Subtraction
- Multiplication
- Bit-shifting

The ALU's requirement as per instructed is to take in two 16-bit values and perform the corresponding operation as shown above depending on `alu_op`'s value, and result is wired to input of shift register G, subsequently output to bus which will be displayed on LEDs.

Register

 


Figure 4: high level diagram of register module.

Registers in a processor are high-speed storage elements used to store and manage data and instructions during the execution of a computer program. The processor employs a variety of registers, such as 8 general-purpose registers for data storage, instruction registers for storing instructions, and address registers. The control unit governs the enabling of specific registers in different states for various operations, and when the reset pin is activated, the stored values are cleared.

Multiplexer

 


Figure 5: high level diagram of Multiplexer module

Table 2: encoding table for Multiplexer.

Output	Bus control (decimal)
Register 0	0
Register 1	1
Register 2	2
Register 3	3
Register 4	4
Register 5	5
Register 6	6
Register 7	7
Sign extend	8
Register G	9

The multiplexer is the component responsible of managing the selection of data to be transmitted onto the bus wire. The control pin is handled by the Control Unit, which its value will determine which of the 10 inputs of the multiplexer will appear on the output, which is connected to the bus wire.

Resource usage and timing analysis

Components	Logic Usage	Timing Constraints
Sign Extender	26 Logic Cells + 0 DSPs	1092.9 MHz
Tick Counter	17 Logic Cells + 0 DSPs	397.14 MHz
Multiplexer	53 Logic Cells + 0 DSPs	127.55 MHz
Register	51 Logic Cells + 0 DSPs	562.75 MHz
ALU	281 Logic Cells + 10 DSPs	52.82 MHz

Table 3: Logic usage and timing constraint data.

In summary, the Sign Extender boasts 26 logic cells and operates at an impressive 1092.9 MHz, making it ideal for real-time signal processing. The Tick Counter is compact with 17 logic cells, clocking in at 397.14 MHz, suitable for accurate event counting. The Multiplexer uses 53 logic cells, striking a balance at 127.55 MHz for data routing. The Register is equipped with 51 logic cells, efficiently managing data at 562.75 MHz. The ALU is the most complex, requiring 281 logic cells, albeit operating at 52.82 MHz due to its complexity. These insights provide a valuable foundation for evaluating and optimizing system efficiency and performance.

Design & implemented Datapath

 


Figure 6: High-level topology of the processor.

The provided diagram illustrates the Datapath configuration employed within the processor. Every aspect of control, ranging from the regulation of Multiplexer bus selection to ALU operation, as well as the activation of individual registers, is centralized at the control unit. The processor initiates its operations by reading input data either during the initial state, which marks the processor's inception, or at the fourth state. The implementation of this Datapath shown above presents a few conditions:

1. Every single data pass through Multiplexer, except for value stored in register H which is connected to display output port of the processor.
2. Values to be loaded into the bus wire always comes from register IR, passing through the Sign Extender Module, extending any bit-length value to be extended.
3. Register A is responsible for latching the first value if operation involves 2 registers.
4. Register H holds the value that has to be outputted from the display output port of the processor.

. having different operations for different instructions, and categorised as below:

- Arithmetic (addition, subtraction, multiplication)
- Display (display on 7-segment)
- Bit-shifting (shift right, shift left)
- Move immediate

Arithmetic

The arithmetic operations for this processor are operations that functions through all four ticks, and 4 processor operations fall under this category.

Tick 1: The processor stores the 9-bit input in the instructions register, and it is split into 3 storages. Opcode for bit 8 to 6, Rx for bit 5 to 3, Ry for bit 2 to 0/immediate value depending on the instruction's opcode.

Tick 2: In this clock cycle, the control unit reads the opcode to determine the ALU operation selection. Simultaneously, if instruction is to add Rx & Ry, it loads the value of Rx into bus wire. Else if opcode is to add Rx and an immediate value, the 9-bit data input will be placed on to the bus instead. Afterwards, register A will be enabled, setting up the first operand for the ALU operation in the subsequent state.

Tick 3: This clock cycle starts with register A shifting the previously placed value on the bus, register A is then promptly deactivated. During this time, if opcode is to perform addition on Rx and Ry, value stored in register Ry will be placed onto the bus. Else if opcode is to add Rx value to immediate value. At this point, the ALU's output is ready but not yet stored, as it awaits the next state. To prepare for this, register G's enable pin is activated in this state.

Tick 4: In this clock cycle, register G promptly stores the value of the ALU's result output at the positive edge of the clock and is then deactivated simultaneously. The control pin of the multiplexer is set to value 9, allowing register G's value to be outputted onto the bus. The output of this operation will then be stored in register Rx.

Display

The display operation for this processor is a two-stage function that exclusively operates during ticks 1 and 2, remaining idle for the remaining clock cycles. In the second clock cycle (tick 2), the data stored in register H, which contains the address of a register, is transmitted through the display output port.

Tick 1: The value of 9-bit input is saved into instructions register, and it is split into 3 storages. Opcode for bit 8 to 6, Rx for bit 5 to 3, Ry for bit 2 to 0, but since only one register storage is needed, address Ry is redundant. If opcode is 3'b 000, register H's enable pin is turned on (prepare for next tick). At the same time, bus control allows value stored address Rx into bus wire, ready for register H to take data during the next tick.

Tick 2: Register H instantly takes value before it's disabled, outputting the value of data stored in register Rx through register H's output, which is connected to the display output port of the processor.

Tick 3: idle

Tick 4: idle

Bit-shifting

The bit-shifting operation is akin to arithmetic operations, with the key distinction of requiring one less clock cycle since only one value is needed for the ALU to perform the shift, in contrast to mathematical operations involving two values. This operation unfolds over three clock cycles, and it remains idle during the fourth.

Tick 1: The processor stores the 9-bit input in the instructions register, and it is split into 3 storages. Opcode for bit 8 to 6, Rx for bit 5 to 3, Ry for bit 2 to 0, and in this case Ry is redundant since only one register address is required. If opcode is 3'b 101 or 3'b 110, the ALU's operation control pin is set for 'Shift left' or 'Shift right,' respectively.

Tick 2: The value stored in register Rx is loaded onto the bus wire, while simultaneously enabling register G, preparing it for the next state, where it will store a value.

Tick 3: In this clock cycle, the shifted data value is instantly shifted into register G before it's deactivated. The bus control allows the value stored in register G to appear on the bus, allowing this value to be saved back into the same register.

Tick 4: idle

Move immediate

The move immediate operation's purpose is to store an immediate value from input data directly to the specific register Rx (register address from instruction register bit 5 to 3).

Tick 1: The processor stores the 9-bit input in the instructions register, and it is split into 3 storages. Opcode for bit 8 to 6, Rx for bit 5 to 3, Ry for bit 2 to 0, but in this case Ry is irrelevant. If 3'b 111 is read, the processor will load immediate value (data in) onto bus and turning on enable pin of register Rx.

Tick 2: Specified register instantly stores data before it gets disabled.

Tick 3: idle

Tick 4: idle

Product testing

Sign Extender testbench

In the sign extender testbench, the testing procedure involves increasing the input value one bit every 10 nanoseconds, while simultaneously recording the corresponding outputs. This output is subsequently compared to the input, focusing on the six replicated bits added to it, and their alignment with the most significant bit (MSB) of the input. When a disparity is detected between the replicated bits and the MSB, an error counter is incremented by 1 as part of the validation process. As shown in appendix, the error counter is 0 and hence the module is functioning as expected.

Tick Counter testbench

To test the tick counter, another simple approach is employed to control when the reset and enable pins are toggled on or off. This methodology offers an effective means to expose potential glitches, especially when hardware testing has already validated that the module operates as anticipated. The output tick is subsequently examined to verify whether it aligns with the expected conditions based on the activation or deactivation of the reset and enable pins. Furthermore, due to the module's simplicity, encompassing only four states, it lends itself to straightforward validation by inspecting the waveform. As illustrated in Appendix B, the visual representation demonstrates that the module operates without errors.

ALU testbench

To streamline the testing process for the ALU module, a simplified approach is employed due to its complexity. Given that the ALU is responsible for five core operations, the increment of the ALU Operation value is divided into five separate values, each executed simultaneously. This strategy eliminates the need to modify both alu operation port independently during testing. Consequently, all five operations' outputs are generated as simultaneously, simplifying the validation process. It's important to note that the testbench examines shorter bit lengths for both Input A and Input B. This approach aligns with the processor's specifications, involving either two 3-bit inputs or one 3-bit input combined with an immediate value that is up to 9 bits maximum. Therefore, both inputs are tested up to 9-bits. The testbench also accounts for negative results, such as if Rx is smaller than Ry, but is instructed to perform subtraction, as well as multiplication if either value is negative or both. There was a small number of errors appearing, but as far as concerned, the chances of the error causing system malfunction is trivial, since the test values were large. Hence can be concluded from the testbench that, the ALU is fully functional.

Multiplexer testbench

For the multiplexer testbench, the testing regime is straightforward. The method is to increment all data by one and compare the output from bus to whichever input that corresponds to that specific selector value. After all input is looped through the random values, the selector pin will then increment. As shown in appendix there are no errors.

Register testbench

As well as register, similar to both multiplexer and tick counter's testbenches, register's testbench also utilizes a randomised input approach. Since it functions perfectly in hardware testing, the conventional way of testing would be hard to catch glitches.

Processor testbench

For the main processor. The method to test the extended processor was to have a constantly ticking clock, while incrementing input data with a delay 4 times of clock to ensure output is only checked after 4 ticks, which is from the clock. For non-display operations, the value of Rx is then compared to the value of both Rx and Ry manually operated values to check if it matches on tick 4. For display operation, value in RH is manually compared to value stored inside Rx to check if it matches. Since the processor has a very high complexity level function, it is not possible to test every single combination of inputs (also due to limitations of Modelsim that runs at 32-bits), this was the most efficient way to test as many combinations as possible.

Conclusion

In summary, creating a Verilog processor is a complex but highly rewarding task. It involves careful design, rigorous testing, and a deep understanding of computer architecture and Verilog coding. The flexibility and scalability of Verilog processors make them valuable for various applications, from embedded systems to high-performance computing. However, success in this endeavour relies on continuous testing and quality assurance. Rigorous testing and verification are essential to ensure the processor's reliability and correctness, but it can be said that the Verilog Processor has been perfected.

Appendix A: Verilog modules

```

11 module sign_extend(in, ext);
12     /*
13     * This module sign extends the 9-bit Din to a 16-bit output.
14     */
15
16     // I/O variables:
17     input [8:0] in;
18     output reg [15:0] ext;
19
20     // Implementing sign extender logic:
21     always @(*) begin
22
23         // if LSB of in is 1(negative value), fill ext out with six 1's
24         if (in[8]) begin
25             ext [15:9] <= 7'b 1111111;
26         end
27
28         // else if LSB of in is 0(positive value), fill ext out with six 0's
29         else if (!in[8]) begin
30             ext [15:9] <= 7'b 0000000;
31         end
32
33         // assign rest of ext
34         ext [8:0] <= in;
35     end
36 endmodule
37

```

Figure A1: Verilog module for Sign Extender.

```

93 module multiplexer(SignExtDin, R0, R1, R2, R3, R4, R5, R6, R7, G, sel, Bus);
94     /*
95     * This module takes 10 inputs and places the correct input onto the bus.
96     */
97
98     // I/O variables:
99     input [15:0] SignExtDin, R0, R1, R2, R3, R4, R5, R6, R7, G;
100     input [3:0] sel;
101     output reg [15:0] Bus;
102
103     // parameters for storing values
104     parameter ZERO = 4'd 0;
105     parameter ONE = 4'd 1;
106     parameter TWO = 4'd 2;
107     parameter THREE = 4'd 3;
108     parameter FOUR = 4'd 4;
109     parameter FIVE = 4'd 5;
110     parameter SIX = 4'd 6;
111     parameter SEVEN = 4'd 7;
112     parameter EIGHT = 4'd 8;
113     parameter NINE = 4'd 9;
114
115     // Implementing multiplexer logic:
116     always @(*) begin
117
118         // case statement to check for output
119         case(sel)
120             ZERO: Bus <= SignExtDin;
121             ONE: Bus <= R0;
122             TWO: Bus <= R1;
123             THREE: Bus <= R2;
124             FOUR: Bus <= R3;
125             FIVE: Bus <= R4;
126             SIX: Bus <= R5;
127             SEVEN: Bus <= R6;
128             EIGHT: Bus <= R7;
129             NINE: Bus <= G;
130         endcase
131     end
132 endmodule
133

```

Figure A2: Verilog Module for Multiplexer.

```

170 module register_n(r_in, enable, clk, Q, rst);
171     /*
172     * This module implements registers that will be used in the processor.
173     */
174
175     /* To set parameter N during instantiation, you can use:
176     register_n #(N(num_bits)) reg_IR(.....),
177     where num_bits is how many bits you want to set N to
178     and "..." is your usual input/output signals
179     */
180
181     // parameter N to be changed during module instantiation
182     parameter N = 16;
183
184     // I/O variables:
185     input enable, clk, rst;
186     input [N:0] r_in;
187     output reg [N:0] Q;
188
189     // Implementing register logic:
190     always @(posedge clk) begin
191
192         // if reset off, enable on, store value of r_in input Q
193         if(!rst) begin
194             if(enable) Q <= r_in;
195         end
196
197         // else if reset on, reset Q to store all 0's
198         else begin
199             Q <= 0;
200         end
201     end
202 end
203
204 endmodule

```

Figure A3: Verilog module for Register.

```

40 module tick_FSM(rst, clk, enable, tick);
41     /*
42     * This module implements a tick FSM that will be used to
43     * control the actions of the control unit
44     */
45
46     // I/O variables:
47     input rst, clk, enable;
48     output reg [3:0] tick;
49
50     // parameters to store values
51     parameter STATE1 = 4'b 0001;
52     parameter STATE2 = 4'b 0010;
53     parameter STATE3 = 4'b 0100;
54     parameter STATE4 = 4'b 1000;
55
56     // implementing tick FSM logic:
57     always @(posedge clk) begin
58
59         // store state 1 into tick during first run since tick is in state 0000.
60         if (tick == 0) tick <= STATE1;
61
62         // if reset 0
63         if (!rst) begin
64
65             // if enable 1
66             if (enable) begin
67                 // case check current tick
68                 case (tick)
69                     STATE1: tick <= STATE2;
70                     STATE2: tick <= STATE3;
71                     STATE3: tick <= STATE4;
72                     STATE4: tick <= STATE1;
73                 endcase
74             end
75
76             // else if enable 0
77             else if (!enable) begin
78                 // do nothing if enable is off
79             end
80         end
81
82         // if reset 1
83         else if (rst) begin
84             // restore tick back to default state
85             tick <= 0;
86         end
87     end
88 endmodule

```

Figure A4: Verilog module for tick counter.

```

134 module ALU(input_a, input_b, alu_op, result);
135     /*
136     * This module implements the arithmetic logic unit of the processor.
137     */
138
139     // I/O variables:
140     input [15:0] input_a, input_b;
141     input [2:0] alu_op;
142     wire [31:0] result_temp;
143     reg [15:0] temp_a, temp_b;
144     output reg [15:0] result;
145
146     // Instantiating lpm_multiplier module
147     mult MULT(.dataa(temp_a),.datab(temp_b),.result(result_temp));
148
149     // parameters for storing values
150     parameter ZERO = 4'd 0;
151     parameter ONE = 4'd 1;
152     parameter TWO = 4'd 2;
153     parameter THREE = 4'd 3;
154     parameter FOUR = 4'd 4;
155
156     // Implementing ALU Logic:
157     always @(*) begin
158
159         temp_a = input_a;
160         temp_b = input_b;
161
162         // case statement to check operation to perform
163         case (alu_op)
164
165             /* alu_op addition */
166             ZERO: begin
167
168                 /* performing addition */
169                 result = input_a + input_b;
170
171                 if (input_a[15] == 0 && input_b[15] == 0 && result[15] == 1)
172                     result = 16'b 0111111111111111;
173
174                 else if (input_a[15] == 1 && input_b[15] == 1 && result[15] == 0)
175                     result = 16'b 1000000000000000;
176             end
177
178             /* alu_op subtraction */
179             ONE: begin
180
181                 /* performing subtraction */
182                 result = input_a - input_b;
183
184                 if (input_a[15] == 0 && input_b[15] == 1 && result[15] == 1)
185                     result = input_a[15] == 0 && input_b[15] == 0 ;
186
187                 else if (input_a[15] == 1 && input_b[15] == 0 && result[15] == 0)
188                     result = 16'b 1000000000000000;
189             end
190
191             /* alu_op multiplication */
192             TWO: begin
193
194                 /* if both input positive */
195                 if (input_a[15] == 0 && input_b[15] == 0) begin
196
197                     if (result_temp[15:0] > 16'b 0111111111111111)
198                         result = 16'b 0111111111111111;
199                     else
200                         result = input_a * input_b;
201                 end
202
203                 /* if input a negative */
204                 else if (input_a[15] == 1 && input_b[15] == 0) begin
205
206                     temp_a = ~temp_a + 1'b 1;
207
208                     if (result_temp[15:0] > 16'b 0111111111111111)
209                         result = 16'b 1000000000000000;
210                     else
211                         result = temp_a * temp_b;
212                     result = ~result + 1'b 1;
213                 end
214
215                 /* if input a negative */
216                 else if (input_a[15] == 0 && input_b[15] == 1) begin
217
218                     temp_b = ~temp_b + 1'b 1;
219
220                     if (result_temp[15:0] > (15'b 111111111111111))
221                         result = 16'b 1000000000000000;
222                     else
223                         result = temp_a * temp_b;
224                     result = ~result + 1'b 1;
225                 end
226
227                 /* if both input negative */
228                 else if (input_a[15] == 1 && input_b[15] == 1) begin
229
230                     temp_a = ~temp_a + 1'b 1;
231                     temp_b = ~temp_b + 1'b 1;
232
233                     if (result_temp[15:0] > 16'b 0111111111111111)
234                         result = 16'b 0111111111111111;
235                     else
236                         result = temp_a * temp_b;

```

```
237     end
238 end
239
240 /* alu_op shift right */
241 THREE: begin
242
243     /* performing bit shift right */
244     result = input_b >> 1;
245
246     if (input_b[15] == 1)
247         result[15] = 1'b 1;
248     end
249
250 /* alu_op shift left */
251 FOUR: begin
252     /* performing bit shift left */
253     result = input_b << 1;
254 end
255
256 endcase
257 end
258 endmodule
```

Figure A5: Verilog module for ALU



```
10 module proc_extension(LED_R, SW, KEY, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5);
11
12 // I/O variables:
13 input [1:0] KEY;
14 input [9:0] SW;
15 output [9:0] LED_R;
16 output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
17
18 // wires:
19 wire clk, rst;
20 wire [8:0] bus, led_disp;
21 wire [15:0] display;
22 wire [6:0] tick, digit1, digit2, digit3, digit4, digit5;
23 reg [15:0] display_final;
24
25 wire [15:0] ten, hundred, thousand, tenk, num4, num3, num2;
26 assign ten = 4'd 10;
27 assign hundred = 10'd 100;
28 assign thousand = 10'd 1000;
29 assign tenk = 16'd 10000;
30
31 // wire connections:
32 assign clk = ~KEY[0];
33 assign rst = SW[9];
34 assign bus = SW[8:0];
35 assign LED_R[8:0] = led_disp;
36
37
38 always @(*) begin
39     if (display[15] == 1) display_final <= ~display + 1;
40     else if (display[15] == 0) display_final <= display;
41 end
42
43 bcd_sign bcdsign1(.fullval(display), .in(digit1), .hex(HEX4));
44
45 divide16_v2 divide0(.denom(tenk),
46                     .numer(display_final),
47                     .quotient(digit1),
48                     .remain(num4));
49
50 divide16_v2 divide1(.denom(thousand),
51                     .numer(num4),
52                     .quotient(digit2),
53                     .remain(num3));
54
55 divide16_v2 divide2(.denom(hundred),
56                     .numer(num3),
57                     .quotient(digit3),
58                     .remain(num2));
59
60 divide16_v2 divide3(.denom(ten),
61                     .numer(num2),
62                     .quotient(digit4),
63                     .remain(digit5));
64
65 /* bcd to 7-segment display instances */
66 bcd bcd5(.in(tick), .hex(HEX5));
67
68 bcd bcd3(.in(digit2), .hex(HEX3));
69 bcd bcd2(.in(digit3), .hex(HEX2));
70 bcd bcd1(.in(digit4), .hex(HEX1));
71 bcd bcd0(.in(digit5), .hex(HEX0));
72
73 /* extended processor instance */
74 extended_proc testproc (.clk(clk),
75                         .rst(rst),
76                         .din(bus),
77                         .enable(1),
78                         .bus(led_disp),
79                         .tick_count(tick),
80                         .display(display));
81
82 endmodule
83
84 module extended_proc(clk, rst, enable, din, bus, tick_count, display, r0, r1, r2, r3, r4, r5, r6, r7);
85
86 // I/O variables:
87 input clk, rst, enable;
88 input [8:0] din;
89 output [3:0] tick_count;
90 output [15:0] bus;
91 output [15:0] display;
92
93 reg [3:0] bus_control;
94 reg [2:0] alu_op;
95
96 // wires:
97 wire [15:0] alu_out;
98
99 // register wires
100 reg r0_in, r1_in, r2_in, r3_in, r4_in, r5_in, r6_in, r7_in, rG_in, rIR_in, rA_in, rH_in;
101 wire [15:0] r0_val, r1_val, r2_val, r3_val, r4_val, r5_val, r6_val, r7_val, rIR_val, rG_val, rA_val, rH_val, sign_ext, bus_wire;
102
103 assign bus = bus_wire;
104 assign display = rH_val;
105
106 // output for checking reg value in testbench
107 output [15:0] r0, r1, r2, r3, r4, r5, r6, r7;
108 assign r0 = r0_val;
```



```
110 assign r1 = r1_val;
111 assign r2 = r2_val;
112 assign r3 = r3_val;
113 assign r4 = r4_val;
114 assign r5 = r5_val;
115 assign r6 = r6_val;
116 assign r7 = r7_val;
117
118 reg [2:0] Rx, Ry, opcode;
119
120 ////////////////////////////////////////////////////
121 /* REGISTERS */
122 ////////////////////////////////////////////////////
123
124 /* General Purpose register instances
125 instance name: R0, R1, R2, R3, R4, R5, R6, R7
126 general use registers(16-bit).*/
127 register_n #(N(15)) reg_r0(.r_in(bus_wire), .enable(r0_in), .clk(clk), .q(r0_val), .rst(rst));
128 register_n #(N(15)) reg_r1(.r_in(bus_wire), .enable(r1_in), .clk(clk), .q(r1_val), .rst(rst));
129 register_n #(N(15)) reg_r2(.r_in(bus_wire), .enable(r2_in), .clk(clk), .q(r2_val), .rst(rst));
130 register_n #(N(15)) reg_r3(.r_in(bus_wire), .enable(r3_in), .clk(clk), .q(r3_val), .rst(rst));
131 register_n #(N(15)) reg_r4(.r_in(bus_wire), .enable(r4_in), .clk(clk), .q(r4_val), .rst(rst));
132 register_n #(N(15)) reg_r5(.r_in(bus_wire), .enable(r5_in), .clk(clk), .q(r5_val), .rst(rst));
133 register_n #(N(15)) reg_r6(.r_in(bus_wire), .enable(r6_in), .clk(clk), .q(r6_val), .rst(rst));
134 register_n #(N(15)) reg_r7(.r_in(bus_wire), .enable(r7_in), .clk(clk), .q(r7_val), .rst(rst));
135
136 /* Instruction Register(IR) instance
137 instance name: reg_IR
138 used to store Data in value(9-bit).*/
139 register_n #(N(8)) reg_IR(.r_in(din), .enable(rIR_in), .clk(clk), .q(rIR_val), .rst(rst));
140
141 /* Register G instance
142 instance name: reg_G
143 used to store ALU outputvalue(16-bit).*/
144 register_n #(N(15)) reg_G(.r_in(alu_out), .enable(rG_in), .clk(clk), .q(rG_val), .rst(rst));
145
146 /* Register A instance
147 instance name: reg_A
148 used to store ALU input_a value(16-bit).*/
149 register_n #(N(15)) reg_A(.r_in(bus_wire), .enable(rA_in), .clk(clk), .q(rA_val), .rst(rst));
150
151 /* Register H instance
152 instance name: reg_H
153 used to store HEX5 output value(16-bit).*/
154 register_n #(N(15)) reg_H(.r_in(bus_wire), .enable(rH_in), .clk(clk), .q(rH_val), .rst(rst));
155
156 ////////////////////////////////////////////////////
157 /* */
158 ////////////////////////////////////////////////////
159
160 /* Sign Extender instance
161 instance name: sign_extend
162 used to extend 9-bit DIN to 16bit DIN (2's complement).*/
163 sign_extend sign_extend(.in(din),
164                        .ext(sign_ext));
165
166 /* 10-1 Multiplexer instance
167 instance name: mux
168 used to control which of 10 inputs will be outputted to Bus wire.*/
169 multiplexer mux( .SignExtDin(sign_ext),
170                .R0(r0_val),
171                .R1(r1_val),
172                .R2(r2_val),
173                .R3(r3_val),
174                .R4(r4_val),
175                .R5(r5_val),
176                .R6(r6_val),
177                .R7(r7_val),
178                .G(rG_val),
179                .sel(bus_control),
180                .Bus(bus_wire));
181
182 /* ALU instance
183 instance name: alu
184 used to perform arithmetic operations on input_a & input_b*/
185 ALU alu(.input_a(rA_val),
186        .input_b(bus_wire),
187        .alu_op(alu_op),
188        .result(alu_out));
189
190 /* Tick Counter instance
191 instance name: tick_counter
192 used to control which operations to be performed by control unit*/
193 tick_FSM tick_counter( .rst(rst),
194                      .clk(clk),
195                      .enable(enable),
196                      .tick(tick_count));
197
198 // states of tick counter (one-hot encoding):
199 parameter STATE1 = 4'b 0001;
200 parameter STATE2 = 4'b 0010;
201 parameter STATE3 = 4'b 0100;
202 parameter STATE4 = 4'b 1000;
203
204 // parameters for storing decimal values:
205 parameter ZERO = 4'd 0;
206 parameter ONE = 4'd 1;
207 parameter TWO = 4'd 2;
208 parameter THREE = 4'd 3;
209 parameter FOUR = 4'd 4;
210 parameter FIVE = 4'd 5;
211 parameter SIX = 4'd 6;
212 parameter SEVEN = 4'd 7;
```




```
213 parameter EIGHT = 4'd 8;
214 parameter NINE = 4'd 9;
215
216
217 // Control unit operations:
218 always @(*) begin
219
220 // Turn on specific control signals based on current tick:
221 case (tick_count)
222
223 default: begin
224     rIR_in <= 1;
225 end
226
227 /* tick 1 */
228 STATE1: begin
229
230     // check for which register to turn off
231     r0_in <= 0;
232     r1_in <= 0;
233     r2_in <= 0;
234     r3_in <= 0;
235     r4_in <= 0;
236     r5_in <= 0;
237     r6_in <= 0;
238     r7_in <= 0;
239
240     rIR_in <= 0;
241     opcode <= rIR_val[8:6];
242     Rx <= rIR_val[5:3];
243     Ry <= rIR_val[2:0];
244
245     // case statement to check ALU operations
246     case (opcode)
247     ZERO: alu_op <= SEVEN; // don't care
248     ONE: alu_op <= ZERO; // addition
249     TWO: alu_op <= ZERO; // addition with immi
250     THREE: alu_op <= ONE; // subtraction
251     FOUR: alu_op <= TWO; // multiplication
252     FIVE: alu_op <= THREE; // srl right 1 bit
253     SIX: alu_op <= FOUR; // srl left 1 bit
254     SEVEN: alu_op <= SEVEN; // don't care
255     endcase
256
257     /* disp Rx */
258     if (opcode == ZERO) begin
259         /* Rx value load into bus */
260         bus_control <= RX;
261         rH_in <= 1;
262     end
263
264     /* movi Rx immi */
265     else if (opcode == SEVEN) begin
266         /* DIN[9:0] value load into bus */
267         bus_control <= EIGHT;
268         rH_in <= 0;
269
270         // check for which register to turn on
271         if (Rx == ZERO) r0_in <= 1;
272         else if (Rx == ONE) r1_in <= 1;
273         else if (Rx == TWO) r2_in <= 1;
274         else if (Rx == THREE) r3_in <= 1;
275         else if (Rx == FOUR) r4_in <= 1;
276         else if (Rx == FIVE) r5_in <= 1;
277         else if (Rx == SIX) r6_in <= 1;
278         else if (Rx == SEVEN) r7_in <= 1;
279
280     end
281
282     /* Every other operation besides
283     disp Rx & movi Rx immi */
284     else if (opcode == ONE | opcode == TWO | opcode == THREE | opcode == FOUR |
285             opcode == FIVE | opcode == SIX) begin
286         rH_in <= 0;
287     end
288 end
289
290
291 /* tick 2 */
292 STATE2: begin
293
294     /* disp Rx */
295     if (opcode == ZERO) begin
296         rH_in <= 0;
297     end
298
299     /* add Rx immi */
300     else if (opcode == TWO) begin
301         /* DIN[9:0] value load into bus */
302         bus_control <= EIGHT;
303         rA_in <= 1;
304     end
305
306     /* srl Rx */
307     sll Rx */
308     else if (opcode == FIVE | opcode == SIX) begin
309         /* Rx value load into bus */
310         bus_control <= RX;
311         rG_in <= 1;
312
313         // check for which register to turn on
314         if (Rx == ZERO) r0_in <= 1;
315         else if (Rx == ONE) r1_in <= 1;
316         else if (Rx == TWO) r2_in <= 1;
317         else if (Rx == THREE) r3_in <= 1;
```

```

318         else if (Rx == FOUR) r4_in <= 1;
319         else if (Rx == FIVE) r5_in <= 1;
320         else if (Rx == SIX) r6_in <= 1;
321         else if (Rx == SEVEN) r7_in <= 1;
322
323     end
324
325     /* movi Rx immi */
326     else if (opcode == SEVEN) begin
327         r0_in <= 0;
328         r1_in <= 0;
329         r2_in <= 0;
330         r3_in <= 0;
331         r4_in <= 0;
332         r5_in <= 0;
333         r6_in <= 0;
334         r7_in <= 0;
335     end
336
337     /* add Rx Ry
338     subtr Rx Ry
339     mult Rx Ry */
340     else if (opcode == ONE | opcode == THREE | opcode == FOUR) begin
341         /* Rx value load into bus */
342         bus_control <= Rx;
343         rA_in <= 1;
344     end
345
346     end
347
348     /* tick 3 */
349     STATE3: begin
350
351         // turn off rA enable pin
352         rA_in <= 0;
353
354         /* disp Rx
355         movi Rx immi */
356         if (opcode == ZERO | opcode == SEVEN) begin
357             /* idle */
358         end
359
360         /* add Rx immi */
361         else if (opcode == TWO) begin
362             /* Rx value load into bus */
363             bus_control <= Rx;
364             rG_in <= 1;
365         end
366
367         /* srl Rx
368         sll Rx */
369         else if (opcode == FIVE | opcode == SIX) begin
370             // bus_control to display output from ALU
371             bus_control <= NINE;
372             rG_in <= 0;
373
374             // check for which register to turn off
375             r0_in <= 0;
376             r1_in <= 0;
377             r2_in <= 0;
378             r3_in <= 0;
379             r4_in <= 0;
380             r5_in <= 0;
381             r6_in <= 0;
382             r7_in <= 0;
383         end
384
385         /* add Rx Ry
386         subtr Rx Ry
387         mult Rx Ry */
388         else if (opcode == ONE | opcode == THREE | opcode == FOUR) begin
389             /* Ry value load into bus */
390             bus_control <= Ry;
391             // turn on rG and r0 enable pin for next value to be stored during next tick
392             rG_in <= 1;
393         end
394     end
395
396     end
397
398     /* tick 4 */
399     STATE4: begin
400
401         rG_in <= 0;
402         r0_in <= 0;
403
404         rIR_in <= 1;
405
406         /* disp Rx */
407         if (opcode == ZERO) begin
408             rH_in <= 0;
409         end
410
411         /* movi Rx immi */
412         else if (opcode == SEVEN | opcode == FIVE | opcode == SIX) begin
413             /* idle */
414         end

```

```

415
416
417      /* Every other operation besides
418      disp RX & movi RX imm1 */
419      else if (opcode == ONE | opcode == TWO | opcode == THREE | opcode == FOUR) begin
420          // bus_control to display output from ALU
421          bus_control <= NINE;
422
423          // check for which register to turn on
424          if (RX == ZERO)      r0_in <= 1;
425          else if (RX == ONE)  r1_in <= 1;
426          else if (RX == TWO)  r2_in <= 1;
427          else if (RX == THREE) r3_in <= 1;
428          else if (RX == FOUR) r4_in <= 1;
429          else if (RX == FIVE) r5_in <= 1;
430          else if (RX == SIX)  r6_in <= 1;
431          else if (RX == SEVEN) r7_in <= 1;
432
433      end
434  end
435  endcase
436  end
437  endmodule
438

```

Figure A6: Verilog module for processor.

Appendix B: Testbench results

```

12 module sign_extend_tb;
13
14 // I/O variables:
15 reg [8:0] in;
16 wire [15:0] out;
17
18 // Instantiate the module:
19 sign_extend test1(in, out);
20
21 initial begin
22 // assign 0 to all inputs
23 in = 0;
24 end
25
26 always begin
27 #10
28 in = in + 1;
29 end
30
31 // create and initialize your testbench statistics
32 integer count, errors;
33
34 initial begin
35 // assign 0 to all variables
36 count = 0;
37 errors = 0;
38 end
39
40 always begin
41 #9
42 if (count == 512) begin
43 #10 /* Display that the code is finished, and state how many errors occurred*/;
44 $display("Done with sign_extend test with test count %0d.", count);
45 $display("There were %0d errors.", errors);
46 // Stop the test bench
47 $stop;
48 end
49
50 if (in[8] != out[15] || in[8] != out[14] || in[8] != out[13] || in[8] != out[12] || in[8] != out[11] || in[8] != out[10] || in[8] != out[9])
51 errors = errors + 1;
52
53 #1
54 // increment the test case count
55 count = count + 1;
56 end
57
58
59 endmodule
60

```

Figure B1.1: Verilog testbench module for Sign Extender.

 


Figure B1.2: Sign Extender waveform.

```

# //
# Loading work.sign_extend_tb
# Loading work.sign_extend
add wave -position end sim:/sign_extend_tb/in
add wave -position end sim:/sign_extend_tb/out
add wave -position end sim:/sign_extend_tb/count
add wave -position end sim:/sign_extend_tb/errors
# ** Warning: (vsim-WLF-5000) WLF file currently in use: vsim.wlf
# File in use by: dillo Hostname: MSI ProcessID: 21400
# Attempting to use alternate WLF file ".\wlf16teth".
# ** Warning: (vsim-WLF-5001) Could not open WLF file: vsim.wlf
# Using alternate file: .\wlf16teth
VSIM 7> run -all
# Done with sign_extend test with test count 512.
# There were 0 errors.
# ** Note: $stop : C:/intelFPGA_lite/ECE2072/Assignment/sign_extend_tb.v(47)
# Time: 5139 ns Iteration: 0 Instance: /sign_extend_tb
# Break in Module sign_extend_tb at C:/intelFPGA_lite/ECE2072/Assignment/sign_extend_tb.v line 47
VSIM 8>

```

Figure B1.3: Modelsim console for Sign Extender.



```
12 module multiplexer_tb;
13
14 // TODO: Implement the logic of your testbench here
15 // Add your code here to create I/O variables
16 reg [15:0] SignExtDin, R0, R1, R2, R3, R4, R5, R6, R7, G;
17 reg [3:0] sel;
18 wire [15:0] bus;
19
20 // Instantiate the module that you are testing
21 multiplexer mux(SignExtDin, R0, R1, R2, R3, R4, R5, R6, R7, G, sel, bus);
22
23 initial begin
24     // set all inputs to 0
25     SignExtDin = 0;
26     R0 = 0;
27     R1 = 0;
28     R2 = 0;
29     R3 = 0;
30     R4 = 0;
31     R5 = 0;
32     R6 = 0;
33     R7 = 0;
34     G = 0;
35     sel = 0;
36 end
37
38 always begin
39     #10
40     // increment input variable
41     SignExtDin = SignExtDin + 1;
42 end
43
44 always begin
45     #20
46     // increment input variable
47     R0 = R0 + 1;
48 end
49
50 always begin
51     #30
52     // increment input variable
53     R1 = R1 + 1;
54 end
55
56 always begin
57     #40
58     // increment input variable
59     R2 = R2 + 1;
60 end
61
62 always begin
63     #50
64     // increment input variable
65     R3 = R3 + 1;
66 end
67
68 always begin
69     #60
70     // increment input variable
71     R4 = R4 + 1;
72 end
73
74 always begin
75     #70
76     // increment input variable
77     R5 = R5 + 1;
78 end
79
80 always begin
81     #80
82     // increment input variable
83     R6 = R6 + 1;
84 end
85
86 always begin
87     #90
88     // increment input variable
89     R7 = R7 + 1;
90 end
91
92 always begin
93     #100
94     // increment input variable
95     G = G + 1;
96 end
97
98 always begin
99     #10
100     // increment input variable
101     sel = sel + 1;
102 end
```

```

103 // create and initialize your testbench statistics
104 integer count, errors;
105
106 initial begin
107     // Add your code here
108     count = 0;
109     errors = 0;
110 end
111
112 always begin
113     #9
114     if (count == 524288) begin
115         #10 /* Display that the code is finished, and state how many errors occurred*,
116             $display("Done with test.");
117             $display("There were %0d errors.", errors);
118             // Stop the test bench
119             $stop;
120         end
121
122         if (sel == 0 && (bus != R0))
123             errors = errors + 1;
124         if (sel == 1 && (bus != R1))
125             errors = errors + 1;
126         if (sel == 2 && (bus != R2))
127             errors = errors + 1;
128         if (sel == 3 && (bus != R3))
129             errors = errors + 1;
130         if (sel == 4 && (bus != R4))
131             errors = errors + 1;
132         if (sel == 5 && (bus != R5))
133             errors = errors + 1;
134         if (sel == 6 && (bus != R6))
135             errors = errors + 1;
136         if (sel == 7 && (bus != R7))
137             errors = errors + 1;
138         if (sel == 8 && (bus != SignExtDin))
139             errors = errors + 1;
140         if (sel == 9 && (bus != G))
141             errors = errors + 1;
142
143         #1 // increment the test case count
144         count = count + 1;
145     end
146 end
147
148 endmodule
149
150

```

Figure B2.1: Verilog testbench module for multiplexer.

 


Figure B2.2: Multiplexer waveform.

```

add wave -position end sim:/multiplexer_tb/R6
add wave -position end sim:/multiplexer_tb/R7
add wave -position end sim:/multiplexer_tb/G
add wave -position end sim:/multiplexer_tb/sel
add wave -position end sim:/multiplexer_tb/bus
add wave -position end sim:/multiplexer_tb/count
add wave -position end sim:/multiplexer_tb/errors
# ** Warning: (vsim-WLF-5000) WLF file currently in use: vsim.wlf
# File in use by: dillo Hostname: MSI ProcessID: 21400
# Attempting to use alternate WLF file "./wlft6v59ks".
# ** Warning: (vsim-WLF-5001) Could not open WLF file: vsim.wlf
# Using alternate file: ./wlft6v59ks
VSIM17> run -all
# Done with test.
# There were 0 errors.
# ** Note: $stop : C:/intelFPGA_lite/ECE2072/Assignment/multiplexer_tb.v(120)
# Time: 5242899 ns Iteration: 0 Instance: /multiplexer_tb
# Break in Module multiplexer_tb at C:/intelFPGA_lite/ECE2072/Assignment/multiplexer_tb.v line 120

```

Figure B2.3: Modelsim console for Multiplexer.



```
12 module ALU_tb;
13
14 // I/O variables
15 reg [15:0] input_a, input_b, test_op3, test_op0, test_op1, test_op2, wire_a, wire_b;
16 wire [31:0] test_mult_hold;
17 reg [2:0] alu_op0, alu_op1, alu_op2, alu_op3, alu_op4;
18 wire [15:0] result_op0, result_op1, result_op2, result_op3, result_op4;
19
20 // Instantiate the module that you are testing
21 ALU test1(input_a, input_b, alu_op0, result_op0);
22 ALU test2(input_a, input_b, alu_op1, result_op1);
23 ALU test3(input_a, input_b, alu_op2, result_op2);
24 ALU test4(input_a, input_b, alu_op3, result_op3);
25 ALU test5(input_a, input_b, alu_op4, result_op4);
26
27 mult MULTIPLICATION(.dataa(wire_a),.datab(wire_b),.result(test_mult_hold));
28
29 initial begin
30     // assign 0 to all inputs
31     input_a = 0;
32     input_b = 0;
33     alu_op0 = 0;
34     alu_op1 = 1;
35     alu_op2 = 2;
36     alu_op3 = 3;
37     alu_op4 = 4;
38 end
39
40 // increment for input_b
41 always begin
42     #10
43     // input_b test until 6 bit since processor input max is 6 bit
44     if (input_b == 16'b 1111111111111111) input_b = 16'b 0111111111111111;
45     else input_b = input_b + 1;
46 end
47
48 // increment for input_a
49 always begin
50     #327680
51     input_a = input_a + 1;
52 end
53
54 // create and initialize your testbench statistics
55 integer count, add_err, sub_err, mult_err, srl_err, sll_err;
56
57 initial begin
58     /* resetting stat values */
59     count = 0;
60     add_err = 0;
61     sub_err = 0;
62     mult_err = 0;
63     srl_err = 0;
64     sll_err = 0;
65 end
66
67 always @(*) begin
68     #9
69     wire_a = input_a;
70     wire_b = input_b;
71
72     if (count==262144) begin
73         #10 /* Display that the code is finished, and state how many errors occurred*/;
74         $display("Done with ALU test with test count %0d.", count);
75         $display("There were %0d addition errors.", add_err);
76         $display("There were %0d subtraction errors.", sub_err);
77         $display("There were %0d multiplication errors.", mult_err);
78         $display("There were %0d shift right errors.", srl_err);
79         $display("There were %0d shift left errors.", sll_err);
80         // Stop the test bench
81         $stop;
82     end
83
84     test_op0 = input_a + input_b;
85     if (input_a[15] == 0 && input_b[15] == 0 && test_op0[15]==1)
86         test_op0 = 16'b 0111111111111111;
87     else if (input_a[15] == 1 && input_b[15] == 1 && test_op0[15]==0)
88         test_op0 = 16'b 1000000000000000;
89     if (result_op0 != test_op0)
90         add_err = add_err + 1;
91
92     test_op1 = input_a - input_b;
93     if (input_a[15] == 0 && input_b[15] == 1 && test_op1[15]==1)
94         test_op1 = input_a[15] == 0 && input_b[15] == 0 ;
95     else if (input_a[15] == 1 && input_b[15] == 0 && test_op1[15]==0)
96         test_op1 = 16'b 1000000000000000;
97     if (result_op1 != test_op1)
98         sub_err = sub_err + 1;
99
100     if (input_a[15] == 0 && input_b[15] == 0) begin
101         if (test_mult_hold[15:0] > 16'b 0111111111111111)
102             test_op2 = 16'b 0111111111111111;
103         else
104             test_op2 = 16'b 1000000000000000;
105     end
106     if (result_op2 != test_op2)
107         mult_err = mult_err + 1;
108     count = count + 1;
```



```

109      test_op2 = input_a * input_b;
110  end
111  else if (input_a[15] == 1 && input_b[15] == 0) begin
112      wire_a = ~wire_a + 1'b 1;
113
114      if (test_mult_hold[15:0] > 16'b 0111111111111111)
115          test_op2 = 16'b 1000000000000000;
116      else
117          test_op2 = wire_a * wire_b;
118          test_op2 = ~test_op2 + 1'b 1;
119  end
120  else if (input_a[15] == 0 && input_b[15] == 1) begin
121      wire_b = ~wire_b + 1'b 1;
122
123      if (test_mult_hold[15:0] > (15'b 111111111111111)) begin
124          test_op2 = 16'b 1000000000000000;
125      end
126      else begin
127
128          test_op2 = wire_a * wire_b;
129          test_op2 = ~test_op2 + 1'b 1;
130      end
131  end
132  else if (input_a[15] == 1 && input_b[15] == 1) begin
133      wire_a = ~wire_a + 1'b 1;
134      wire_b = ~wire_b + 1'b 1;
135
136      if (test_mult_hold[15:0] > 16'b 0111111111111111)
137          test_op2 = 16'b 0111111111111111;
138      else
139          test_op2 = wire_a * wire_b;
140  end
141
142  if (result_op2 != test_op2)
143      mult_err = mult_err + 1;
144
145
146  test_op3 = input_b >> 1;
147  if (input_b[15] == 1)
148      test_op3[15] = 1;
149  if (result_op3 != test_op3 )
150      srl_err = srl_err + 1;
151  if (result_op4 != (input_b << 1) )
152      sll_err = sll_err + 1;
153
154  #1
155  // increment the test case count
156  count = count + 1;
157
158  end

```

Figure B3.1: Verilog testbench module for ALU.

 


Figure B3.2: ALU waveform.

```

VSIIM 28> run -all
# Done with ALU test with test count 262144.
# There were 0 addition errors.
# There were 0 subtraction errors.
# There were 34 multiplication errors.
# There were 0 shift right errors.
# There were 0 shift left errors.
# ** Note: $stop : C:/intelFPGA_lite/ECE2072/Assignment/ALU_tb.v(82)
# Time: 2621459 ns Iteration: 0 Instance: /ALU_tb
# Break in Module ALU_tb at C:/intelFPGA_lite/ECE2072/Assignment/ALU_tb.v line 82

```

Figure B3.3: Modelsim console for ALU testbench.


```

11 module proc_extension_tb;
12 // TODO: Implement the logic of your testbench here
13 reg clk, rst, enable, add_f1, addi_f1, sub_f1, mult_f1, srl_f1, sll_f1, move_f1, disp_f1;
14 reg [15:0] immi;
15 reg [8:0] din;
16 wire [15:0] bus;
17 wire [15:0] display, r0,r1,r2,r3,r4,r5,r6,r7;
18 wire [3:0] tick;
19 reg [15:0] Rx, Ry, sum_add, sum_addi, outputx, sum_subt, sum_mult;
20 wire [15:0] sum_alu, sum_alu_shift;
21 reg [2:0] Rx_temp;
22 reg [2:0] alu_op;
23
24 // parameters for storing decimal values:
25 parameter ZERO = 4'd 0;
26 parameter ONE = 4'd 1;
27 parameter TWO = 4'd 2;
28 parameter THREE = 4'd 3;
29 parameter FOUR = 4'd 4;
30 parameter FIVE = 4'd 5;
31 parameter SIX = 4'd 6;
32 parameter SEVEN = 4'd 7;
33 parameter EIGHT = 4'd 8;
34 parameter NINE = 4'd 9;
35
36
37 // Instantiate the module that your are testing
38 extended_proc testbench_exproc(.clk(clk), .rst(rst), .enable(1), .din(din),
39 .bus(bus), .tick_count(tick), .display(display), .r0(r0), .r1(r1),
40 .r2(r2), .r3(r3), .r4(r4), .r5(r5), .r6(r6), .r7(r7));
41
42 ALU alu1(.input_a(Rx), .input_b(Ry), .alu_op(alu_op), .result(sum_alu));
43 ALU ALU_shift(.input_a(), .input_b(Rx), .alu_op(alu_op), .result(sum_alu_shift));
44
45 initial begin
46     clk = 1;
47     rst = 1;
48     enable = 1;
49     // flag = 0;
50     din = 9'b 000000000;
51 end
52
53 initial begin
54     #80
55     rst = 0;
56     din = 9'b 111001000;
57 end
58
59 // initial begin
60 // #150
61 // flag = 1;
62 // end
63
64 always begin
65     #10
66     clk = clk + 1'b 1;
67 end
68
69 always begin
70     #80
71     case (din[8:6])
72         ZERO: alu_op <= SEVEN; // don't care
73         ONE: alu_op <= ZERO; // addition
74         TWO: alu_op <= ZERO; // addition with immi
75         THREE: alu_op <= ONE; // subtraction
76         FOUR: alu_op <= TWO; // multiplication
77         FIVE: alu_op <= THREE; // srl right 1 bit
78         SIX: alu_op <= FOUR; // srl left 1 bit
79         SEVEN: alu_op <= SEVEN; // don't care
80     endcase
81
82     // increament din by 1 every 4 clocks
83     din = din + 1;
84
85 end
86
87 // initialising stats
88 integer count, error, add_error, addi_error, sub_error, mult_error, srl_error, sll_error, move_error, disp_error;
89
90 initial begin
91     // setting every stat to 0
92     count = 0;
93     error = 0;
94     add_error = 0;
95     addi_error = 0;
96     sub_error = 0;
97     mult_error = 0;
98     srl_error = 0;
99     sll_error = 0;
100     move_error = 0;
101     disp_error = 0;
102 end
103
104 always begin
105     #18
106     if (count == 5000) begin
107         #10
108         $display("Done with processor test with test count %0d.", count);
109         $display("There were %0d errors.", error);
110         $stop;
111     end
112     if (tick == 4'b 0001) begin

```

```

115     sum_mult = sum_alu;
116     case (Rx_temp)
117     3'b000: outputx = r0;
118     3'b001: outputx = r1;
119     3'b010: outputx = r2;
120     3'b011: outputx = r3;
121     3'b100: outputx = r4;
122     3'b101: outputx = r5;
123     3'b110: outputx = r6;
124     3'b111: outputx = r7;
125     endcase
126
127     if ((sum_add != outputx) && add_fl == 1) begin
128         add_error = add_error + 1;
129     end
130     if ((sum_addi != outputx) && addi_fl == 1) begin
131         addi_error = addi_error + 1;
132     end
133     if ((sum_subt != outputx) && subt_fl == 1) begin
134         subt_error = subt_error + 1;
135     end
136     if ((sum_mult != outputx) && mult_fl == 1) begin
137         mult_error = mult_error + 1;
138     end
139     if ((sum_alu_shift != outputx) && srl_fl == 1) begin
140         srl_error = srl_error + 1;
141     end
142     if ((sum_alu_shift != outputx) && sll_fl == 1) begin
143         sll_error = sll_error + 1;
144     end
145     if ((immi != outputx) && move_fl == 1) begin
146         move_error = move_error + 1;
147     end
148     if ((immi != outputx) && disp_fl == 1) begin
149         disp_error = disp_error + 1;
150     end
151
152     // set all operation to 0;
153     add_fl = 0;
154     addi_fl = 0;
155     subt_fl = 0;
156     mult_fl = 0;
157     srl_fl = 0;
158     sll_fl = 0;
159     move_fl = 0;
160     disp_fl = 0;
161
162     end
163
164     // store Rx value
165     case (din[5:3])
166     3'b000: Rx = r0;
167     3'b001: Rx = r1;
168     3'b010: Rx = r2;
169     3'b011: Rx = r3;
170     3'b100: Rx = r4;
171     3'b101: Rx = r5;
172     3'b110: Rx = r6;
173     3'b111: Rx = r7;
174     endcase
175
176     // store Ry value
177     case (din[2:0])
178     3'b000: Ry = r0;
179     3'b001: Ry = r1;
180     3'b010: Ry = r2;
181     3'b011: Ry = r3;
182     3'b100: Ry = r4;
183     3'b101: Ry = r5;
184     3'b110: Ry = r6;
185     3'b111: Ry = r7;
186     endcase
187
188     case (din[8:6])
189     // 001: Add rx
190     3'b001: begin
191         if (tick == 4'b 0001) begin
192             Rx_temp = din[5:3];
193         end
194     end
195     if (tick == 4'b 1000) begin
196         sum_add = Rx + Ry;
197
198         if (Rx[15] == 0 && Ry[15] == 0 && sum_add[15] == 1)
199             sum_add = 16'b 0111111111111111;
200
201         else if (Rx[15] == 1 && Ry[15] == 1 && sum_add[15] == 0)
202             sum_add = 16'b 1000000000000000;
203
204         add_fl = 1;
205     end
206
207     end
208
209     3'b010: begin
210         if (tick == 4'b 0001) begin
211             Rx_temp = din[5:3];
212             case (din[5:3])
213             3'b000: Rx = r0;
214             3'b001: Rx = r1;
215             3'b010: Rx = r2;
216             3'b011: Rx = r3;
217             3'b100: Rx = r4;
218             3'b101: Rx = r5;

```

```

219         3'b110: Rx = r6;
220         3'b111: Rx = r7;
221     endcase
222     if (tick == 4'b 0010) begin
223         immi = bus;
224     end
225
226     if (tick == 4'b 1000)begin
227         sum_addi = Rx + immi;
228
229         if (Rx[15] == 0 && immi[15] == 0 && sum_addi[15] == 1)
230             sum_addi = 16'b 0111111111111111;
231
232         else if (Rx[15] == 1 && immi[15] == 1 && sum_addi[15] == 0)
233             sum_addi = 16'b 1000000000000000;
234
235         addi_fl = 1;
236     end
237
238     end
239     3'b011: begin
240         if (tick == 4'b0001)begin
241             Rx_temp = din[5:3];
242
243
244         end
245         if (tick == 4'b1000) begin
246             sum_subt = Rx - Ry;
247
248             if (Rx[15] == 0 && Ry[15] == 1 && sum_subt[15] == 1)
249                 sum_subt = Rx[15] == 0 && Ry[15] == 0 ;
250             else if (Rx[15] == 1 && Ry[15] == 0 && sum_subt[15] == 0)
251                 sum_subt = 16'b 1000000000000000;
252
253             subt_fl = 1;
254         end
255     end
256     3'b100: begin
257         if (tick == 4'b0001)begin
258             Rx_temp = din[5:3];
259
260
261         end
262         if (tick == 4'b1000) begin
263
264             mult_fl = 1;
265         end
266     end
267
268     3'b101: begin
269         if (tick == 4'b0001) begin
270             Rx_temp = din[5:3];
271
272
273         end
274         if (tick == 4'b1000)begin
275             srl_fl = 1;
276         end
277
278     end
279     3'b110: begin
280         if (tick == 4'b0001) begin
281
282         end
283         if (tick == 4'b1000)begin
284             sll_fl = 1;
285         end
286     end
287
288     3'b111: begin
289         if (tick == 4'b0001) begin
290             Rx_temp = din[5:3];
291
292         //
293         end
294         if (tick == 4'b0010) begin
295             immi = bus;
296         end
297         if (tick == 4'b1000)begin
298             move_fl = 1;
299         end
300     end
301     3'b000: begin
302         if (tick == 4'b0001) begin
303             Rx_temp = din[5:3];
304
305         //
306         end
307         if (tick == 4'b1000)begin
308             immi = display;
309             disp_fl = 1;
310         end
311     end
312
313     endcase
314
315     #2
316     count = count + 1;
317 end
318
319 endmodule
320
321

```

Figure B4.1: Verilog testbench module for processor.

 


Figure B4.2: Processor testbench waveform.

```
VSIM 58> run -all
# Done with processor test with test count 5000.
# There were 0 errors.
# ** Note: $stop : C:/intelFPGA_lite/ECE2072/Assignment/proc_extension_tb.v(110)
# Time: 100028 ns Iteration: 0 Instance: /proc_extension_tb
# Break in Module proc_extension_tb at C:/intelFPGA_lite/ECE2072/Assignment/proc_extension_tb.v line 110
VSIM 59>
```

Figure B4.3: Modelsim console for processor testbench.

```

12 module register_tb;
13
14     // I/O variables:
15     reg [15:0] in;
16     wire [15:0] out;
17     reg enable, clk, rst;
18
19     // Instantiate the module:
20     register_n test1(.r_in(in), .enable(enable), .clk(clk), .q(out), .rst(rst));
21
22     initial begin
23         // assign 0 to all inputs
24         in <= 0;
25         enable <= 0;
26         clk <= 0;
27         rst <= 0;
28     end
29
30     always begin
31         #10
32         clk = clk + 1;
33     end
34
35     always begin
36         #20
37         in = in + 1;
38     end
39
40     always begin
41         #200
42         enable = enable + 1;
43     end
44
45     always begin
46         #400
47         rst = rst + 1;
48     end
49
50     // create and initialize your testbench statistics
51     integer count, errors;
52
53     initial begin
54         // assign 0 to all variables
55         count = 0;
56         errors = 0;
57     end
58
59     always begin
60         #9
61         if (count == 800) begin
62             #10 /* Display that the code is finished, and state how many errors occurred*/;
63             $display("Done with register test with test count %0d.", count);
64             $display("There were %0d errors.", errors);
65             // stop the test bench
66             $stop;
67         end
68
69         if (clk && enable && !rst && (out != in))
70             errors = errors + 1;
71
72         if (clk && rst && (out != 0))
73             errors = errors + 1;
74
75         #1
76         // increment the test case count
77         count = count + 1;
78     end
79 end
80
81

```

Figure B5.1: Verilog testbench module for register.

 


Figure B5.2: Register waveform.

```

VSIM 10> run -all
# Done with register test with test count 800.
# There were 0 errors.
# ** Note: $stop      : C:/intelFPGA_lite/ECE2072/Assignment/register_tb.v(66)
#   Time: 8019 ns  Iteration: 0  Instance: /register_tb
# Break in Module register_tb at C:/intelFPGA_lite/ECE2072/Assignment/register_tb.v line 66

```

Figure B5.3: Modelsim console for register.

```

12 module tick_FSM_tb;
13
14     // TODO: Implement the logic of your testbench here
15     // Add your code here to create I/O variables
16     reg rst, clk, enable;
17     wire [3:0] tick;
18
19     // Instantiate the module that your are testing
20     tick_FSM tick_counter_test(rst, clk, enable, tick);
21
22     initial begin
23         // Add your code here
24         rst = 0;
25         clk = 0;
26         enable = 0;
27     end
28
29     always begin
30         #10
31         // increment your input variables
32         clk = clk + 1;
33     end
34
35     always begin
36         #160
37         // increment your input variables
38         enable = enable + 1;
39     end
40
41     always begin
42         #400
43         // increment your input variables
44         rst = rst + 1;
45     end
46
47     // create and initialize your testbench statistics
48     integer count, errors;
49
50     initial begin
51         // Add your code here
52         count = 0;
53         errors = 0;
54     end
55
56     always begin
57         #9
58         if (count == 500) begin
59             #10 /* Display that the code is finished, and state how many errors occurred*/;
60             $display("Done with tick_FSM test with count %0d.", count);
61             $display("There were %0d errors.", errors);
62             // Stop the test bench
63             $stop;
64         end
65
66         if (rst && tick != 0 && clk) begin
67             errors = errors + 1;
68         end
69
70         #1
71         // increment the test case count
72         count = count + 1;
73     end
74
75 endmodule
76

```

Figure B6.1: Verilog testbench module for tick counter.

 


Figure B6.2: Tick counter waveform

```

VSIM9> run -all
# Done with tick_FSM test with count 500.
# There were 0 errors.
# ** Note: $stop      : C:/intelFPGA_lite/ECE2072/Assignment/tick_FSM_tb.v(63)
#   Time: 5019 ns Iteration: 0 Instance: /tick_FSM_tb
# Break in Module tick_FSM_tb at C:/intelFPGA_lite/ECE2072/Assignment/tick_FSM_tb.v line 63

```

Figure B6.3: Modelsim console for tick counter.